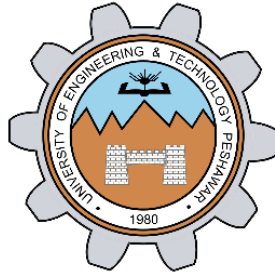


Lab Report : 08



Spring 2020

Electronic Devices and Circuit Theory

Submitted by: **Shah Raza**

Registration No: **18PWCSE1658**

Section: **B**

Submitted to:

Engr. Abdullah Hamid

24th July, 2020.

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

Zener Diode Characteristics

Objectives:

- 1) To study the characteristics of Zener diode.
- 2) To study the voltage regulation in Zener diode regulation circuit.

Equipment:

- ❖ Digital Multimeter (DMM)

Components

- ❖ Zener-Diode: Silicon (1N742A)
- ❖ Resistors: $1K\Omega$, $10K\Omega$, $1M\Omega$
- ❖ Variable Voltage Source

Theory:

Diode:


A diode is a two-terminal electronic component that conducts current primarily in one direction; it has low resistance in one direction, and high resistance in the other.

Zener diode

Zener diode is a P-N junction diode specially designed to operate in the reverse breakdown region. It is acting as normal diode while forward biasing. It has a specific voltage, at which the diode breakdowns while reverse biased. Zener diode damages at the breakdown voltage. But zener diode has a reverse breakdown region.

The basic principle of zener diode is the zener breakdown. When a diode is heavily doped, its depletion region will be narrow. When a high reverse voltage is applied across the junction, there will be a very strong electric field at the junction. And the electron hole pair generation takes place. Thus heavy current flows. This is known as Zener break down.

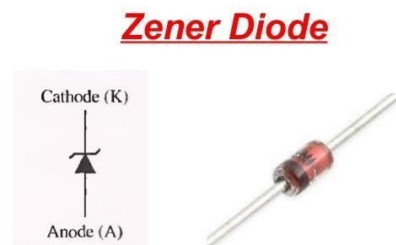So a zener diode, in a forward biased condition, acts as a normal diode. In reverse biased mode, after the breakdown of junction current through the diode increases sharply. But the voltage across it remains constant.




Procedure:


Part A: Zener Diode Characteristics

Construct the circuit of *Fig. 1*. Set the DC supply to 0 V and record the measured value of R.

Circuit Diagram :



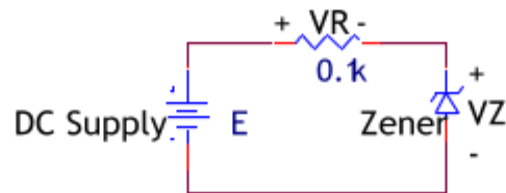



Zener Charactersitic Curve :

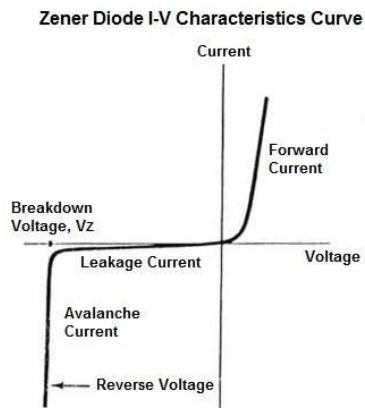

Set the DC supply (E) to the values appearing in Table 4.1 and measure both V_Z and V_R . Calculate the Zener current, I_Z using the Ohm's law given in the table and complete the table.

Circuit Diagram:

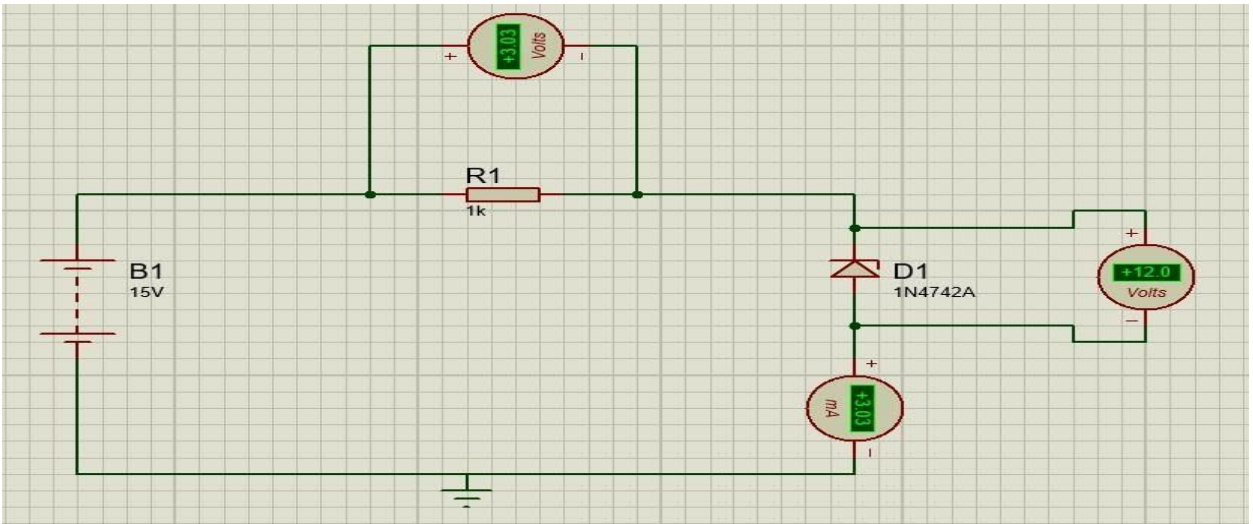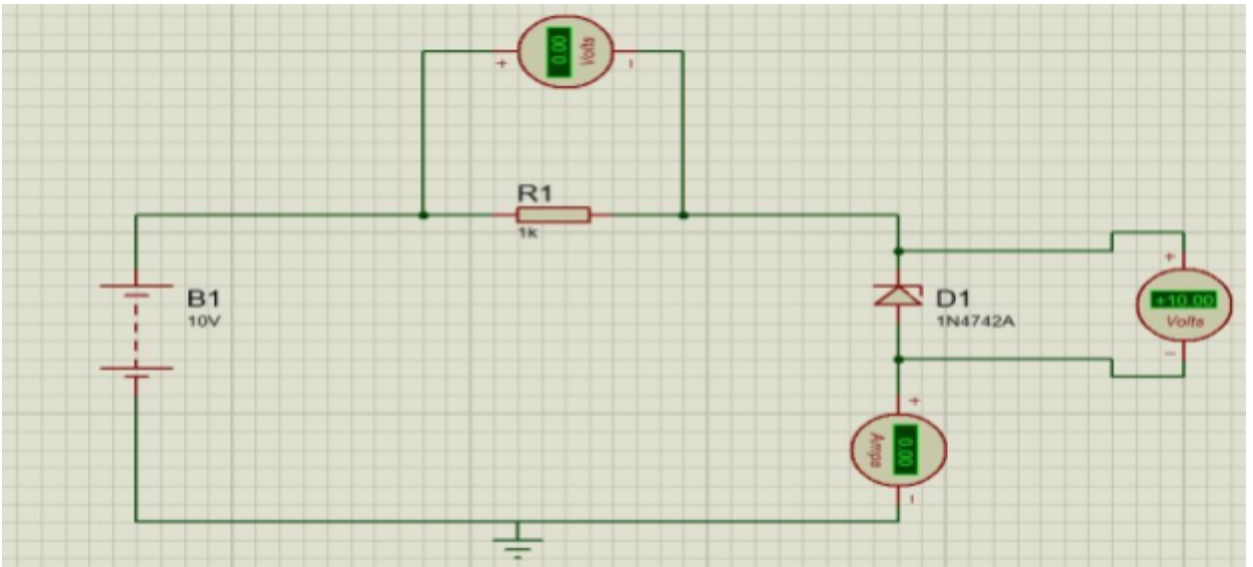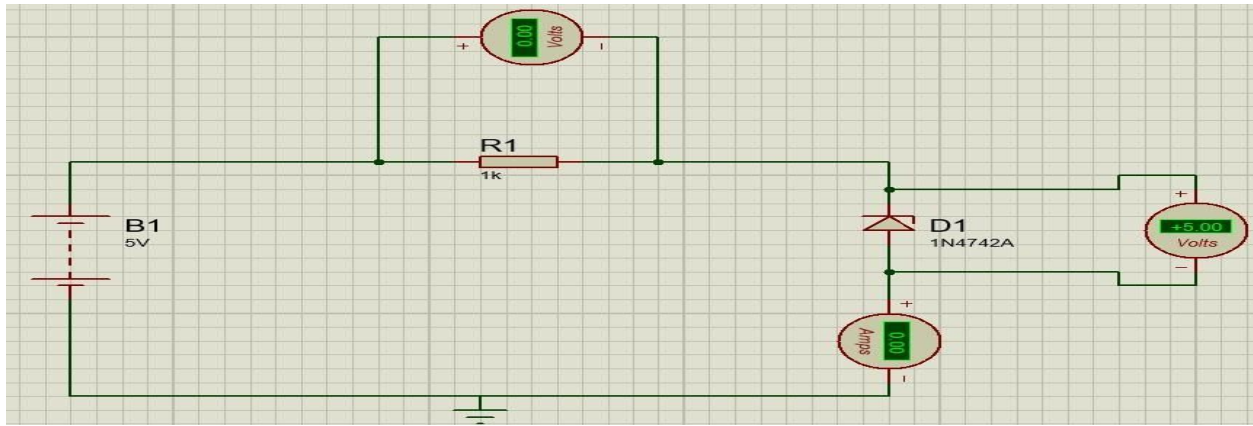

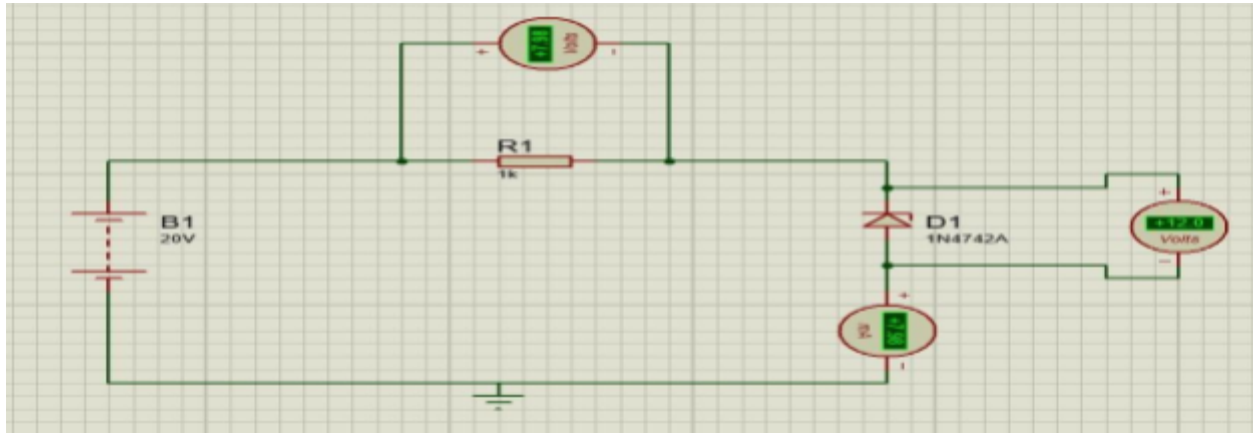


Observations:

S/no	Vcc	Vs(Across Resistor)	Vz	Iz
1	5V	0V	5V	0mA
2	10V	0V	10V	0 mA
3	15V	3.3V	12V	3.03 mA
4	20V	7.98V	12V	7.98 mA



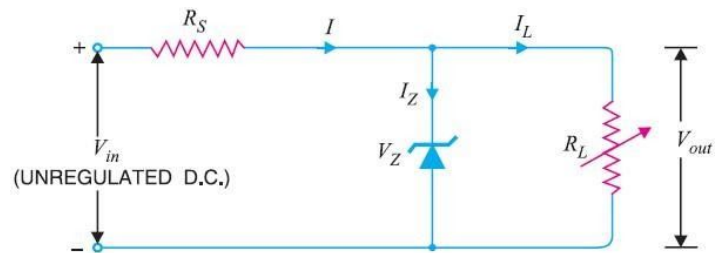
Part B As A Regulator


Construct the circuit of Fig. 2. Record the measured value of each resistor.



Measure the value of V_L and V_R . Using the measured values, calculate the Value for current across R , I_R , current across R_L , I_L , and current across the Zener Diode, I_Z .

Circuit Diagram:

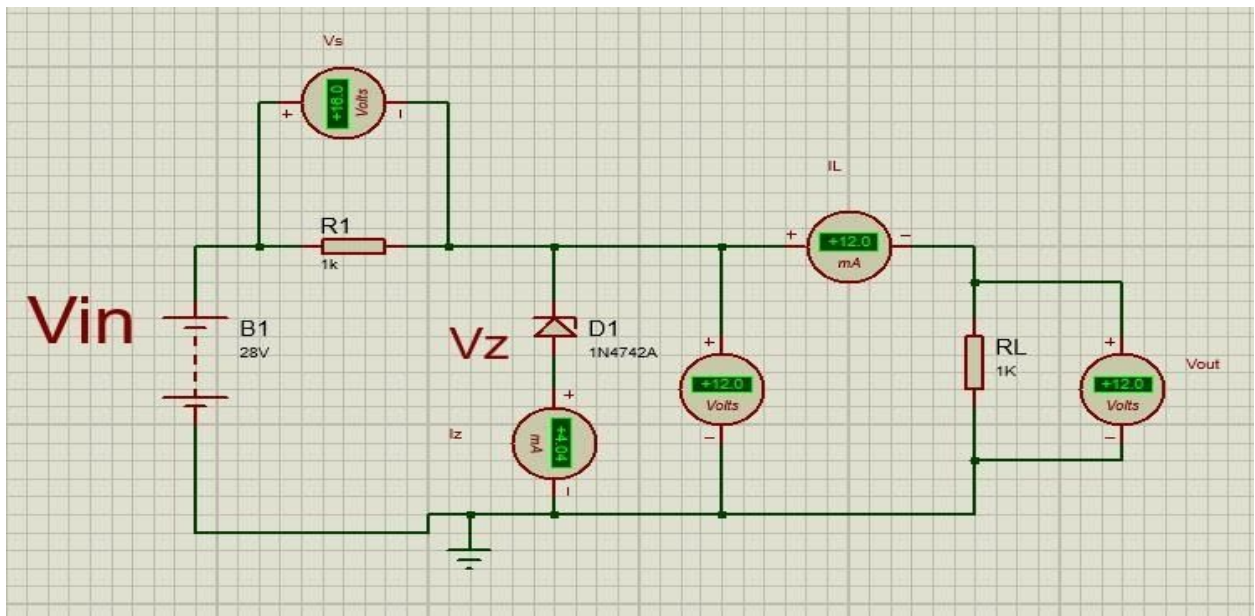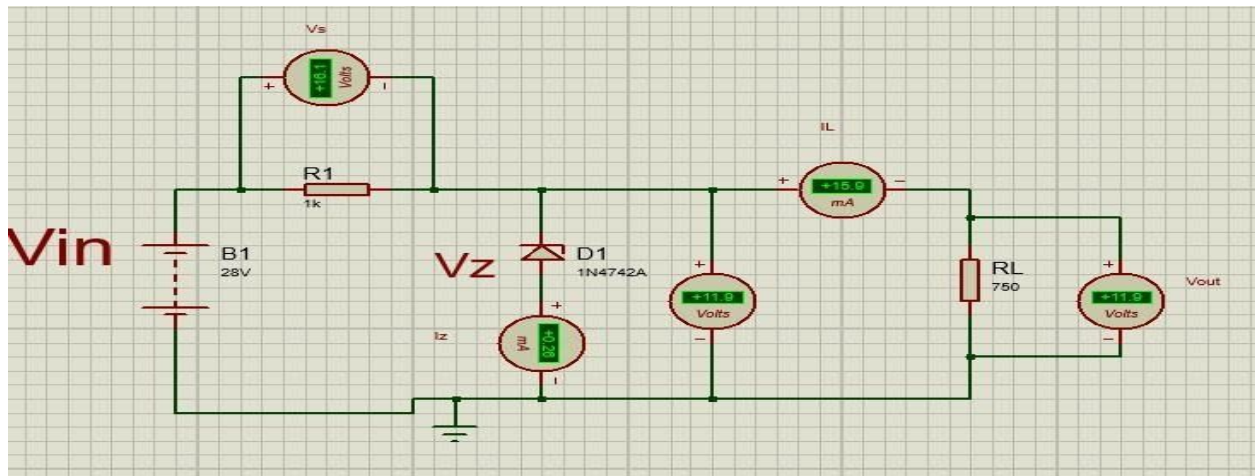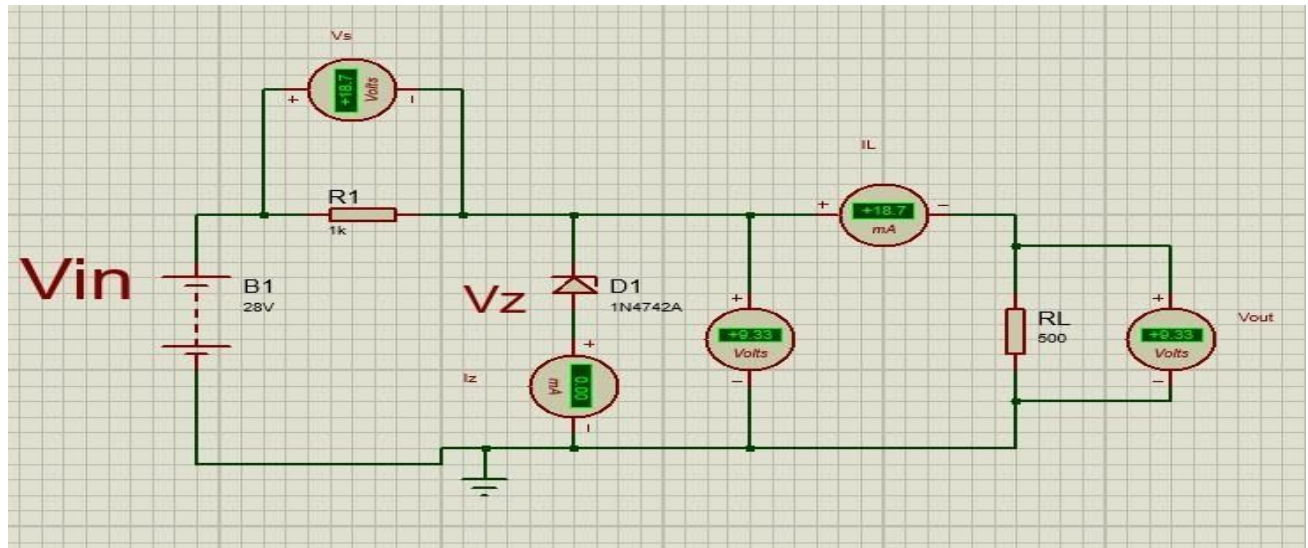

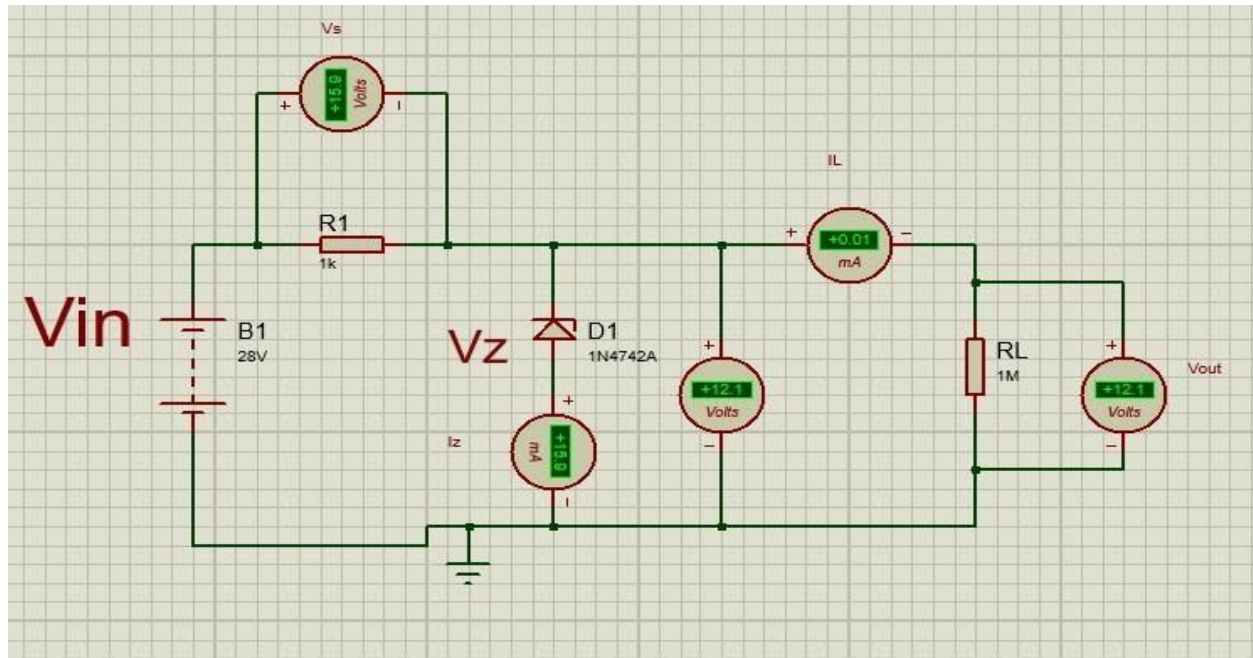

Observations:

S/No	Vin	Vz	Iz	RL	Vout	Vs
1	28V	9.33v	0.00mA	500 _Ω	9.33v	18.7v
2	28V	11.9v	0.28mA	750 _Ω	11.9v	16.1v
3	28V	12v	4.04mA	1k	12v	16v
4	28V	12.1v	15.9mA	1M _Ω	12.1v	15.9v

Conclusion:

The Zener diode, with its accurate and specific reverse breakdown voltage, allows for a simple, inexpensive voltage regulator. Combined with the right resistor, fine control over both the voltage and the supply current can be attained.